


a)

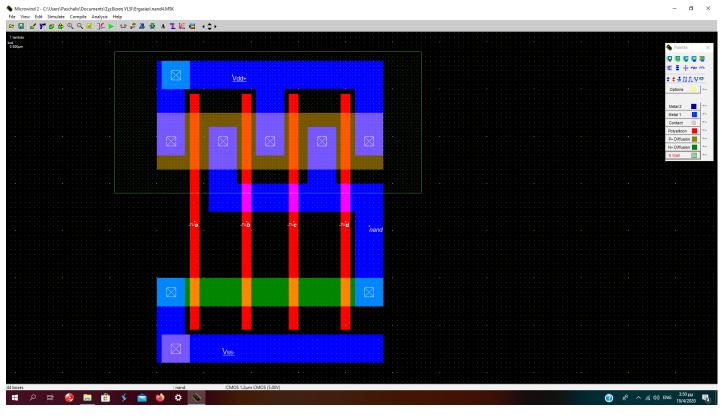


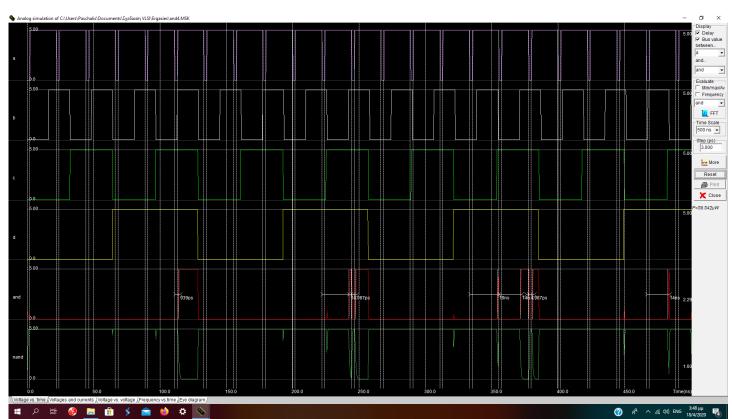

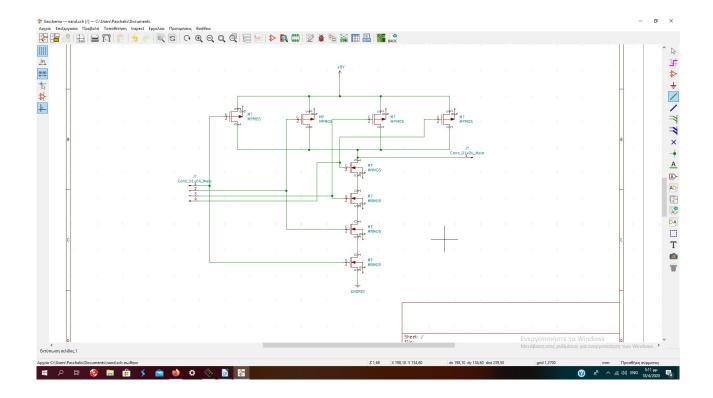

	Inp	outs		outp	uts
a	b	С	d	nand	and
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	1	0	1	0
1	1	1	1	0	1

b)

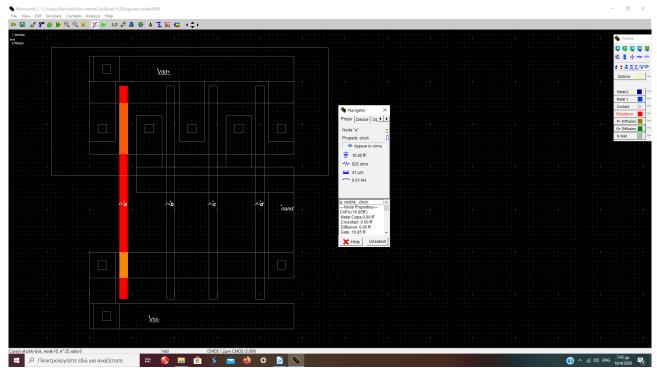


NAND output capatance: 16.85fF

NAND output capatance: 17.08fF


NAND output capatance: 17.08fF


NAND output capatance: 17.08fF

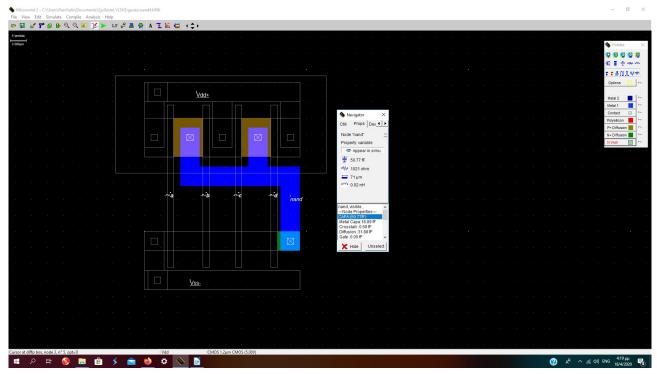


NAND output capatance: 50.77fF



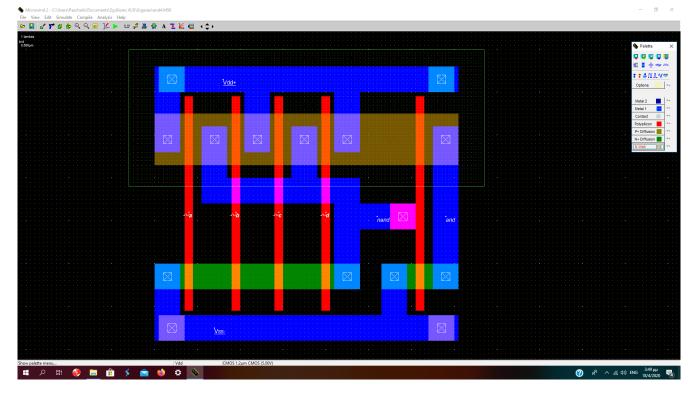


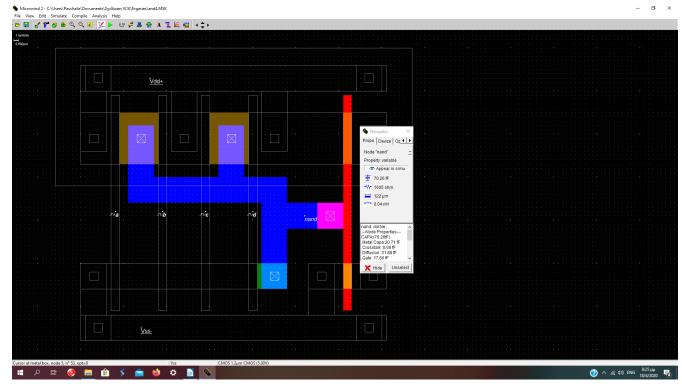


NAND output capatance: 70.26fF

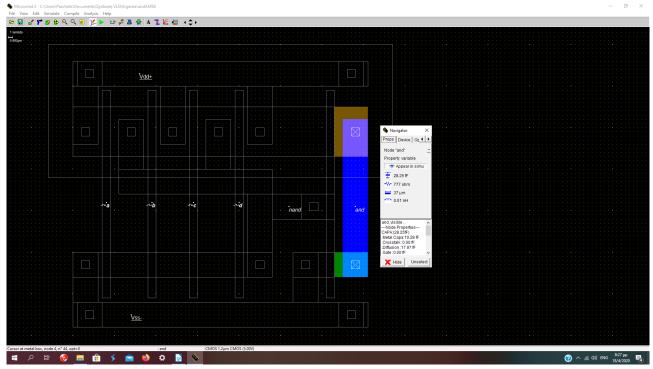


AND output capatance: 26.25fF

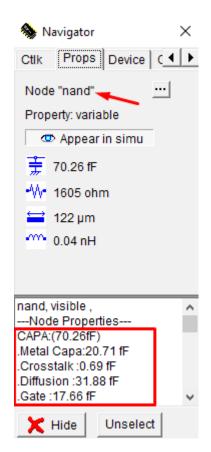

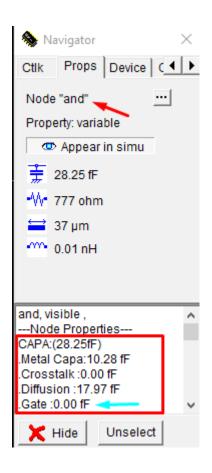




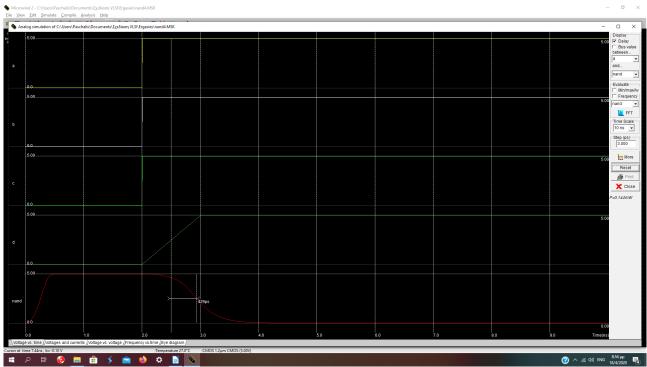

Delay input d-output nand: 429ps


b)

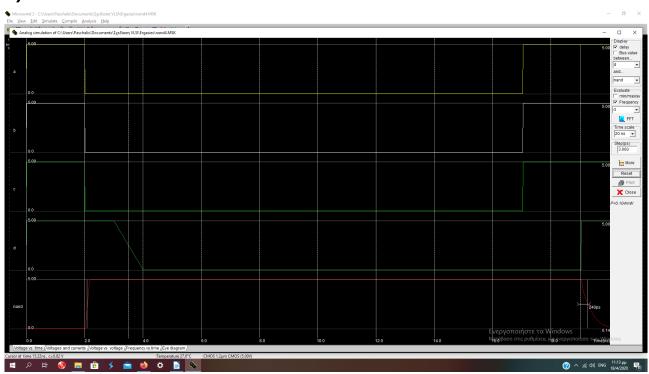


Κατερχόμενες είσοδοι

Delay input a-output nand: 240ps



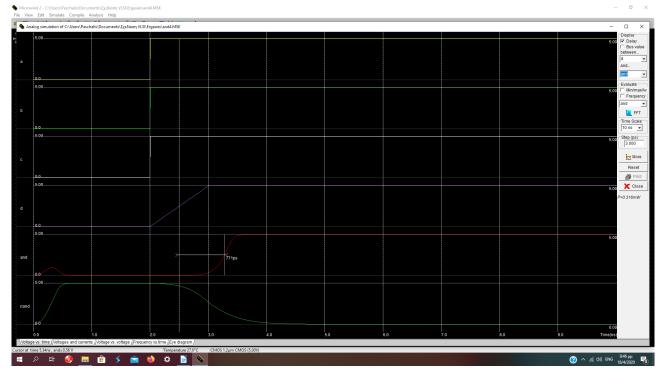

Delay input d-output and: 771ps

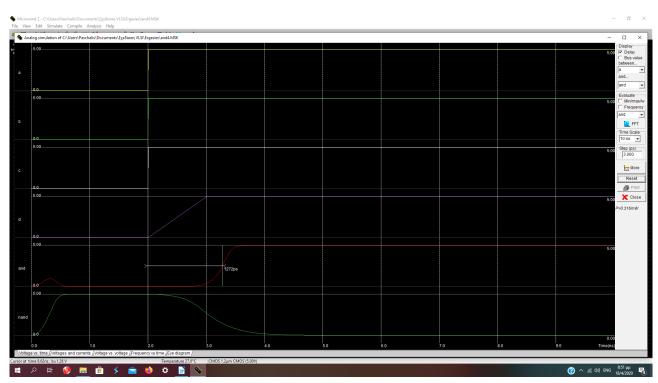

Delay input a-output and: 1272ps


d)Delay between a input and output NAND and AND.

	NAND	AND	NAND inside AND
5 Volt	930 ps	1272 ps	1035 ps
3.5 Volt	1053 ps	1578 ps	1221 ps
2.5 Volt	1290 ps	2157 ps	1569 ps
1.8 Volt	1800 ps	3457 ps	2289 ps
1.2 Volt	3756 ps	9357 ps	4974 ps

5

5.2



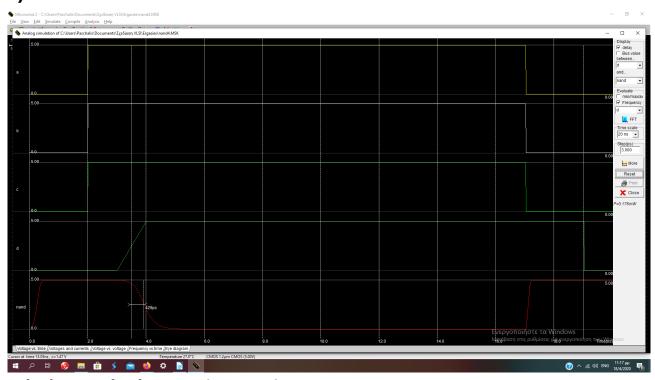

Delay between d and output NAND is 429ps

Time start(ts)=2	Time start(ts)=3
Delay between d and output NAND is 429ps	Delay between d and output NAND is 429ps

